

© 2019 Dr. Kavianpour

*These notes are protected by copy rights.*

*Students are not allowed to reproduce, distribute, sell, or publicly post this course materials without faculty permission*

Final Project  
EECS31L  
Dr. Kavianpour

Use VHDL design a 4-bit ALU (Arithmetic logic Unit) with the 8 instructions:

ADD, REVERSE, MUL, INC, XNOR, NOT, RROTATION, LROTATION.

1-Assume codes for instructions are: 000=ADD, 001=REVERSE, 010=MUL, 011=INC, 100=XNOR, 101=NOT, 110= RROTATION, and 111= LROTATION

2- Assume input numbers are unsigned.

3- For instructions REVERSE, NOT, RROTATION and LROTATION use number  $A_3A_2A_1A_0$

4-For addition result will be in  $C_3C_2C_1C_0$  and carry in CO

4-For multiplication use repeated addition such as  $A+A+A+\dots$  ( B times) and outputs are in  $D_3D_2D_1D_0$ ,  $C_3C_2C_1C_0$  ,

5-Inputs are clock,  $A_3A_2A_1A_0$ ,  $B_3B_2B_1B_0$ , and code for instruction. Output is  $C_3C_2C_1C_0$  and CO in case of add and  $D_3D_2D_1D_0$ ,  $C_3C_2C_1C_0$  in case of multiplication

**Example:**

$A=0111$ ,  $B=0101$ , code=000

Means add  $A+B$  and the result is  $C=0111+0101=1100$  and  $CO=0$

If code is 101

Means NOT of A

$A=0111$ ,  $C=1000$

If code is 001

Means REVERSE

$A=0111$ ,  $C=1110$

If code is 010

Means Multiplication

$A=0111$ ,  $B=0101$ ,

$A * B = 100011$

$D = 0010$

$C = 0011$

**For your report:**

**1-Report**

a--Write if your code is working or partially working

b-Paste Screenshot of simulation results. For 8 instructions for  $A=1000$  and  $B=0111$

c--Paste copy of VHDL file

d-Paste copy of VHDL test bench

**2-Submit VHDL and test bench files**

,