

Lecture 4

Prepared by: Dr. Alireza Kavianpour

How to define a clock

*

* For positive edge triggered :

* **IF(clock'EVENT AND clock = '1') THEN**

* **Q <= '1';**

* ----

* For negative edge triggered :

* **IF(clock'EVENT AND clock = '0') THEN**

* **Q <= '1';**

* ----

VHDL Design for D Flip-Flop

```
* LIBRARY IEEE;
  USE IEEE.std_logic_1164.ALL;

* ENTITY dflipflop IS
  PORT(D :IN BIT; clock :IN BIT; Q :OUT BIT);
  END dflipflop;

* ARCHITECTURE behavior OF dflipflop IS
  BEGIN
    PROCESS(clock)
    BEGIN
      IF(clock'EVENT AND clock = '1') THEN
        IF(D = '1') THEN
          Q <= '1';
        ELSE
          Q <= '0';
        END IF;
      END IF;
    END PROCESS;
  END behavior;
```

VHDL Alternative Description for D Flip-Flop

- * **VHDL Alternative Description for D Flip-Flop Architecture:**

- * **ARCHITECTURE behavior OF dflipflop IS**

BEGIN

PROCESS(clock)

BEGIN

IF(clock'EVENT AND clock = '1') THEN

Q <= D;


END IF;

END PROCESS;

END behavior;


VHDL File for the 74LS74 D Flip-Flop

- * VHDL File for the 74LS74 D Flip-Flop
- * ENTITY dflipflop IS
PORT(D, PRE, CLR, CLOCK :IN BIT; Q,QN :OUT BIT);
END dflipflop;
- * ARCHITECTURE behavior OF dflipflop IS
BEGIN
 PROCESS(**CLOCK, CLR, PRE**)
 BEGIN
 IF CLR = '0' THEN
 Q <= '0'; QN <= '1';
 ELSIF PRE = '0' THEN
 Q <= '1'; QN <= '0';
 ELSIF(**clock'EVENT AND clock = '1'**) THEN
 Q <= D; QN <= NOT D;
 END IF;
 END PROCESS;
END behavior;

 

JK Flip Flop

```
ENTITY jk IS
* PORT( J, K, PRE, CLR, CLOCK :IN BIT; q, qn :INOUT BIT);
* END jk;
* ARCHITECTURE behavior OF jk is
* BEGIN
* PROCESS (CLOCK, CLR, PRE)
* BEGIN IF CLR = '0' THEN
* q <= '0'; qn <= '1'; ELSIF PRE = '0' THEN q <= '1'; qn <= '0';
* ELSIF
* if j = '0' and k = '0' then
* q <= q; qn <= qn;
* elsif j = '1' then
* q <= '1'; qn <= '0';
* elsif k = '1' then
* q <= '0'; qn <= '1';
* elsif j = '1' and k = '1' then
* q <= qn; qn <= q;
* end if;
* end if;
* end process;
* end behavior;
```

 

JK Flip Flop

- * **ENTITY jk IS**
- * **PORT(J, K, PRE, CLR, CLOCK :IN BIT; q, qn :INOUT BIT);**
- * **END jk;**
- * **ARCHITECTURE behavior OF jk is**
- * **BEGIN**
- * **PROCESS (CLOCK, CLR, PRE)**
- * **BEGIN IF CLR = '0' THEN**
- * **q <= '0'; qn <= '1'; ELSIF PRE = '0' THEN q <= '1'; qn <= '0';**
- * **ELSE**
- * **q<= j AND NOT q OR NOT k AND q**
- * **end if;**
- * **end process;**
- * **end behavior;**


Characteristics Equations for Flip flop

- * **SR Flip flop:**
 $q \leq S + \text{NOT } R \text{ AND } q$
- * **JK Flip Flop:**
 $q \leq j \text{ AND NOT } q \text{ OR NOT } k \text{ AND } q$
- * **T Flip flop:**
 $q \leq T \text{ XOR } q$
- * **D Flip flop:**
 $q \leq D$

Registers

- * Registers are nothing more than a group of flip-flops with a common clock.
- * Used to store bits that have a relationship to one another.
- * The most common use of registers is to store bits of numerical data in computers.
- * A 32- or 64-bit machines this simply means that the computers deal with numbers using 32 or 64 bits.
- * During computer operations, such as arithmetic, these numbers must be stored.
- * This storage utilizes registers; in these cases, either 32 or 64 flip-flops with a common clock.

Registers

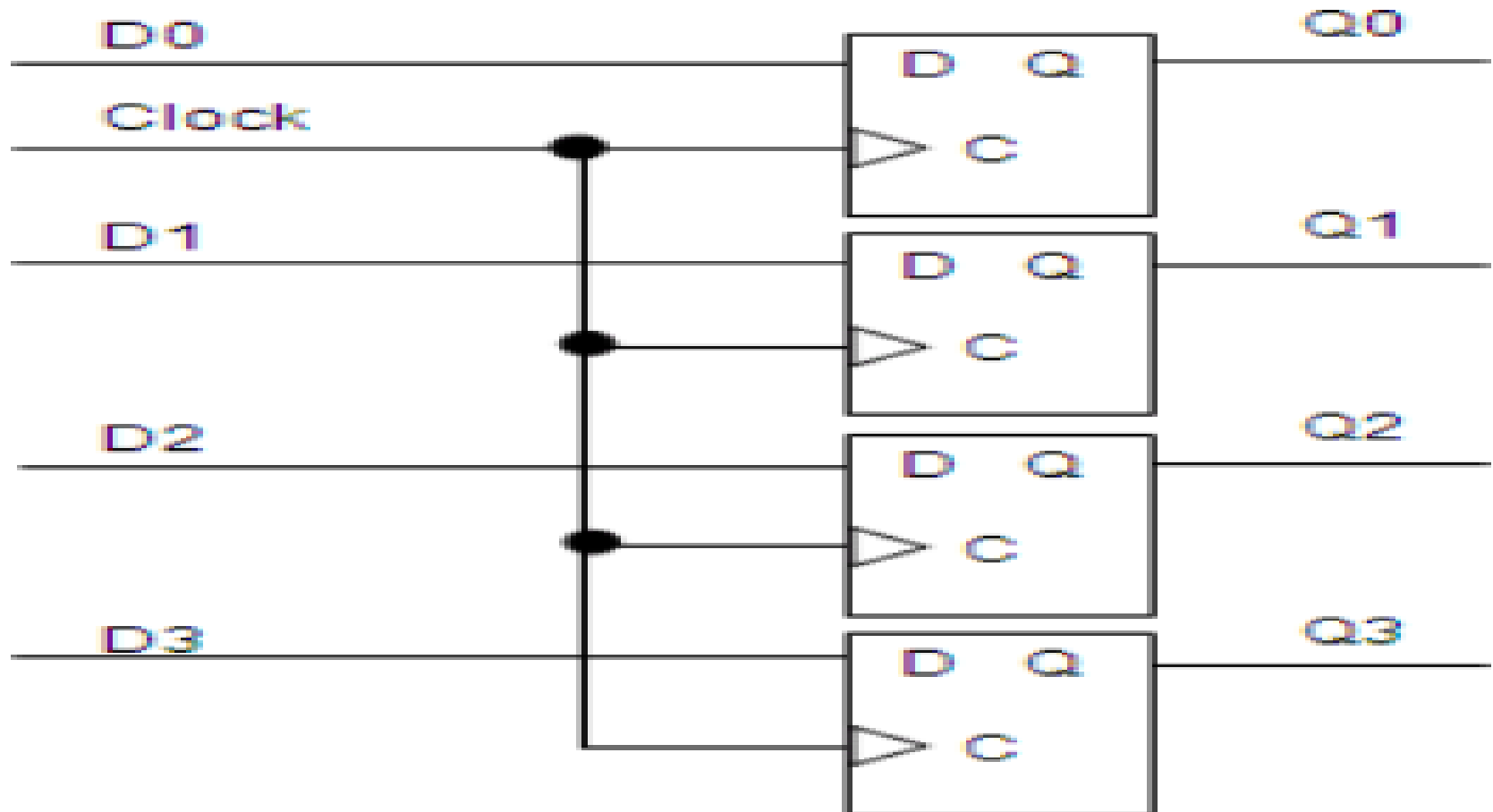

Registers

- * Common examples of registers inside CPU are:
- * PC: program counter
- * SP: stack pointer
- * CCR: condition code register
- * ACC: Accumulator
- * MAR: memory address register
- * MDR: memory data register

VHDL: 4-Bit Register

```
ENTITY register4 IS
PORT(
    CLK          :IN BIT;
    D            :IN BIT_VECTOR(3 DOWNTO 0);
    Q            :OUT BIT_VECTOR(3 DOWNTO 0));
END register4;

ARCHITECTURE behavior OF register4 is
BEGIN
    PROCESS(CLK)
    BEGIN
        IF(CLK'EVENT AND CLK = '1') THEN
            Q <= D;
        END IF;
    END PROCESS;
END behavior;
```



Counter Overview

- * A common example of a MOD 2^N counter can be found in standard clocks and watches.
- * Today, most timekeeping devices are digitally driven with a crystal oscillator running at 32.768 kHz.
- * The reason this value is chosen is because this is an inexpensive configuration for the oscillator and because the value is $1 \text{ Hz} \times 2^5$. This means we need a 15-bit binary counter to produce a 1-second output.


Counter Overview

- * .
- * The clock example points out the limitation of using 2^N counters; namely, that the number of seconds in a minute, minutes in an hour, and hours in a day are not 2^N values. A MOD 60 counter for minutes from seconds, a second MOD 60 counter to get hours from minutes, and a MOD 24 counter to get days from hours.
- * There is another class of digital counters that do not give sequential counts. One example is a Gray code counter.


Ripple Counters

  


Three-Bit Ripple Counter(Asynchronous)

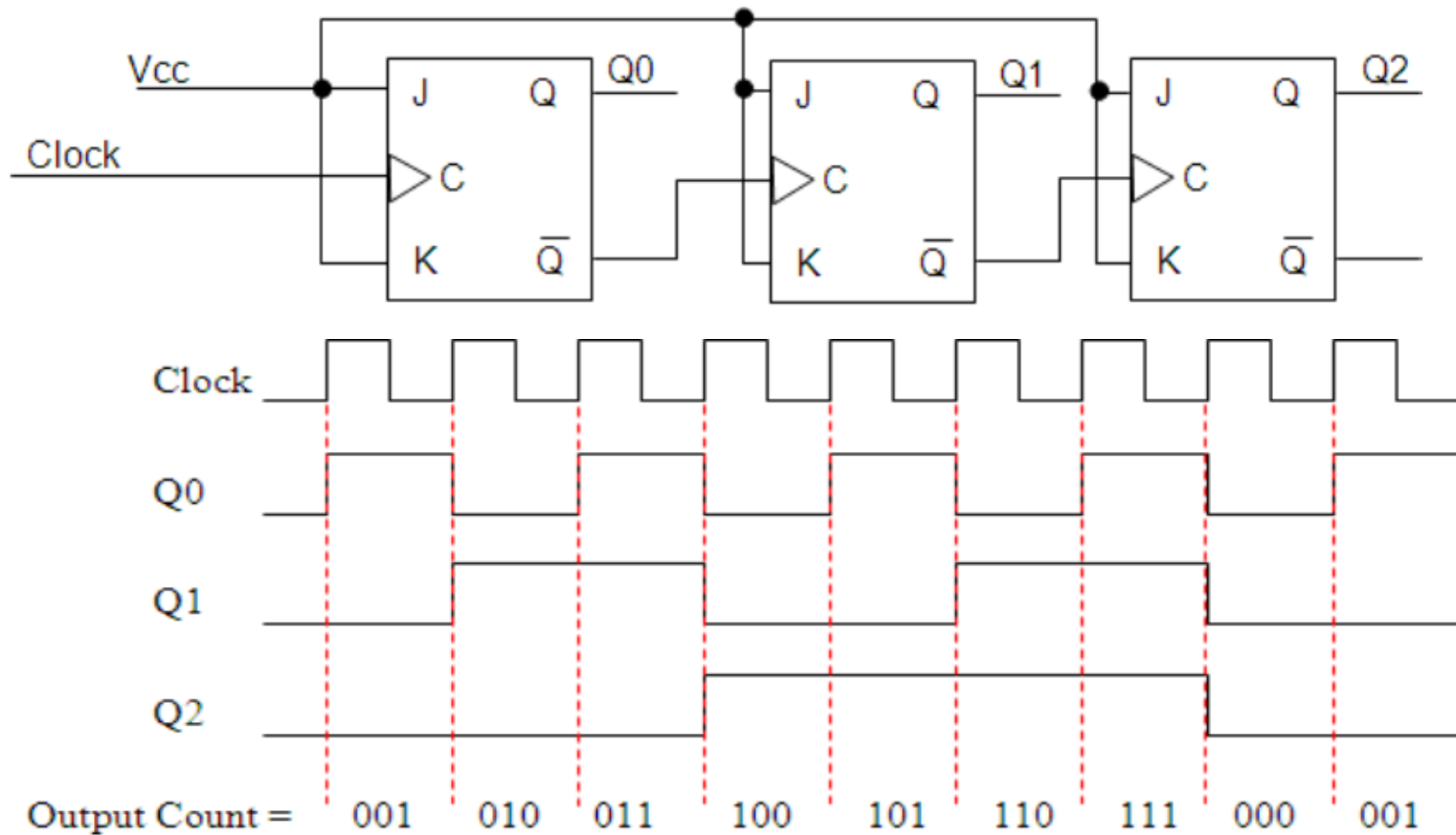

Ripple Counter at 10 kHz

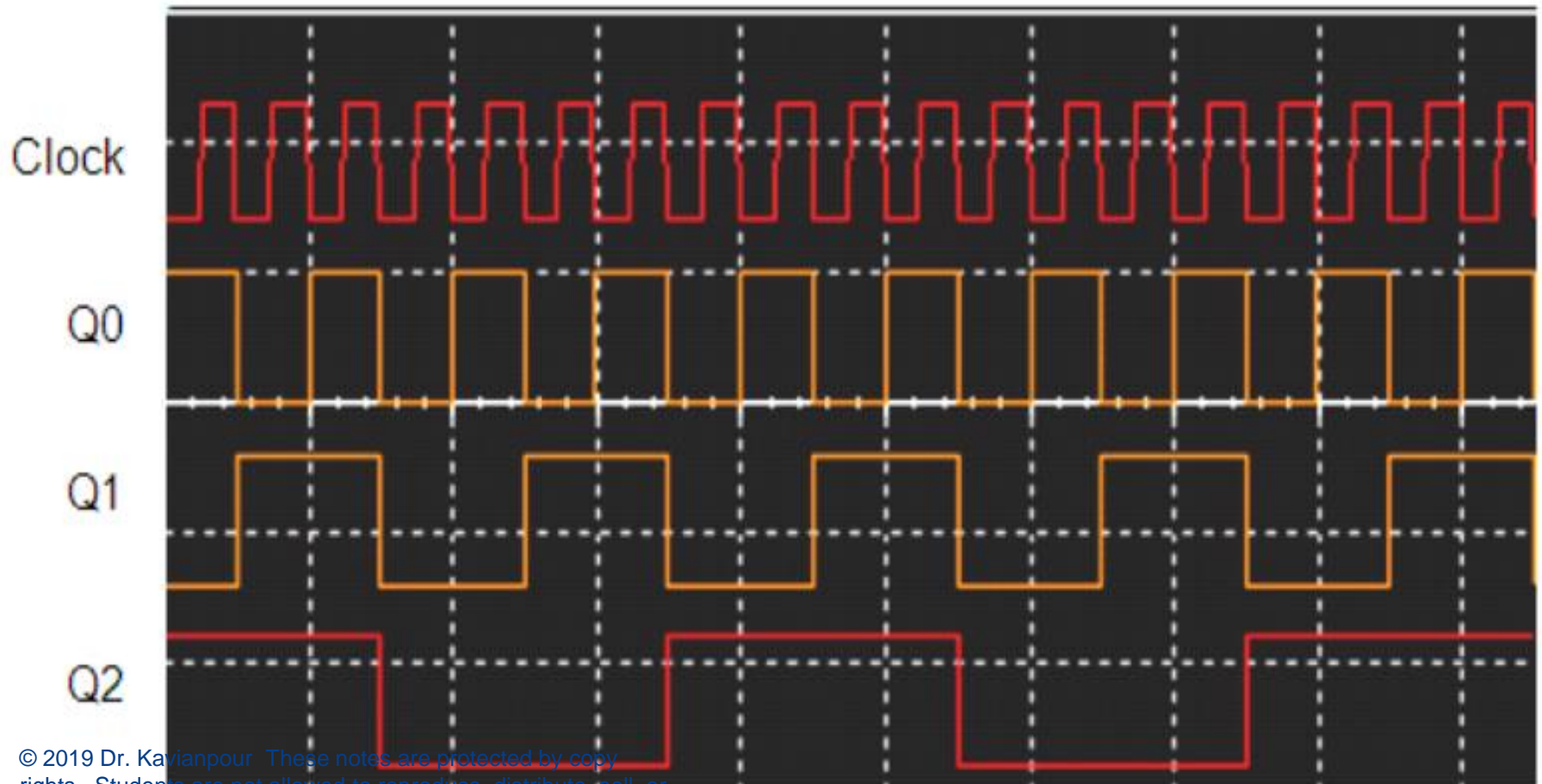

Ripple Counter at 10 MHz

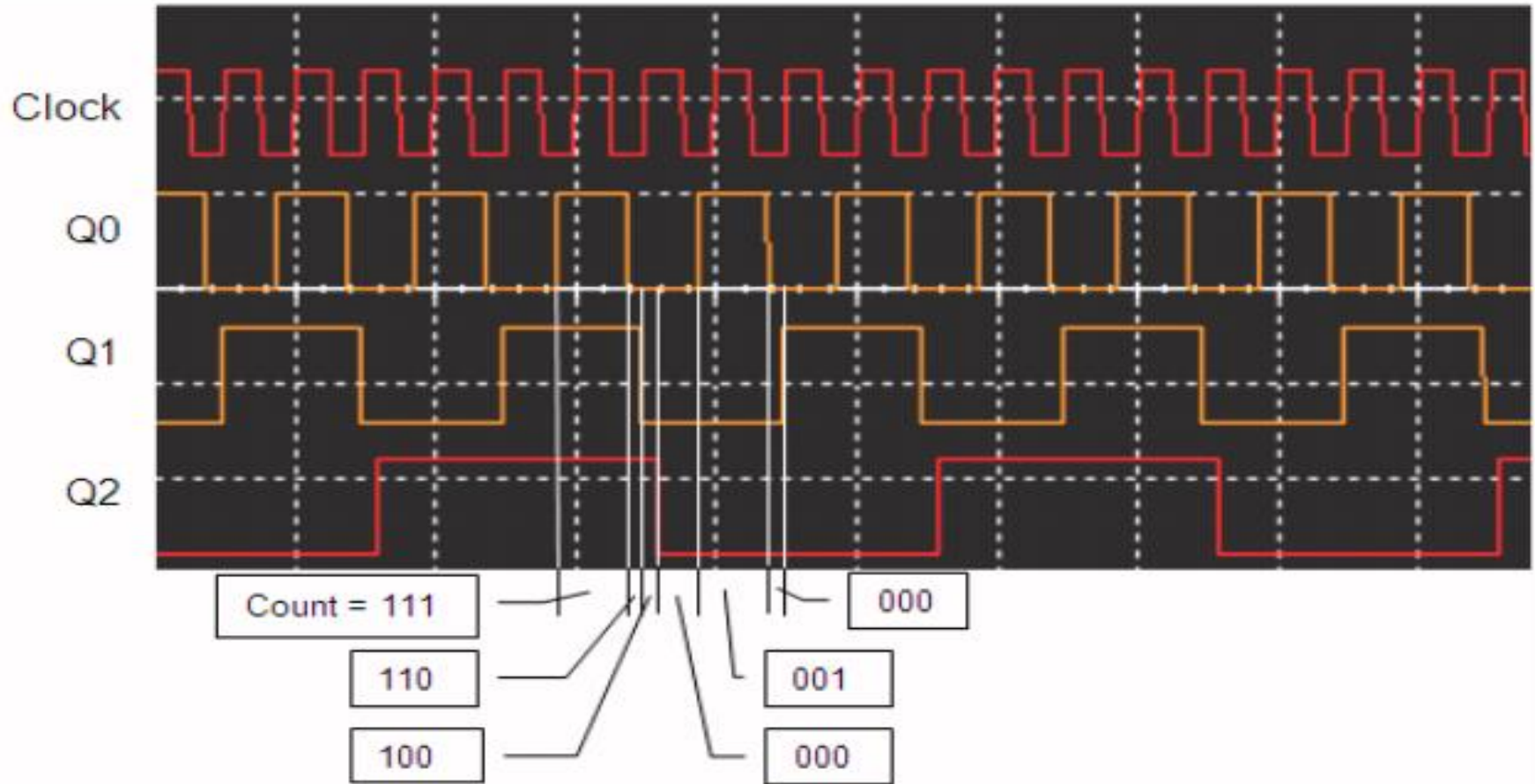

Ripple Count

- * As you can see, the ripple counter does not produce a reliable count sequence at higher frequencies.
- * As shown in the simulation, the counter increments from a count of 111 to a count of 000, but has transition counts of 110 and 100.
- * In a similar fashion, the counter increments from 001 to 010 with a transition count of 000.
- * These transition states at higher frequencies limit the use of ripple counters to applications running at relatively slow speeds, such as time-of-day clocks and watches.

Synchronous Counters


Q2	Q1	Q0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
0	0	0

Changes
each time

Change when
 $Q0 = 1$

Change when
 $Q0 = Q1 = 1$

Synchronous Counter

 

Synchronous Mod-8 Up Counter

```
* ENTITY counter3 IS
PORT(
    CLK :IN BIT;
    Q :BUFFER BIT_VECTOR(2 downto 0));
END counter3;

ARCHITECTURE behavior OF counter3 is
BEGIN
    PROCESS(CLK)
    BEGIN
        IF (CLK'EVENT AND CLK = '1') THEN
            IF Q = "000" THEN Q <= "001";
            ELSIF Q = "001" THEN Q <= "010";
            ELSIF Q = "010" THEN Q <= "011";
            ELSIF Q = "011" THEN Q <= "100";
            ELSIF Q = "100" THEN Q <= "101";
            ELSIF Q = "101" THEN Q <= "110";
            ELSIF Q = "110" THEN Q <= "111";
            ELS Q <= "000";
            END IF;
        END IF;
    END PROCESS;
END behavior;
```

VHDL Counter Description Using INTERER Type

```
* ENTITY counter3 IS
PORT(
    CLK :IN BIT;
    Q :BUFFER INTEGER RANGE 0 TO 7);
END counter3;
ARCHITECTURE behavior OF counter3 is
BEGIN
    PROCESS(CLK)
    BEGIN
        IF (CLK'EVENT AND CLK = '1') THEN
            Q <= Q + 1";
        END IF;
    END PROCESS;
END behavior;
```

MOD-8 Up-Counter With Enable and Clear

```
* ENTITY counter8 IS
PORT(
    CLK :IN BIT;
    CLR,EBL :IN BIT;
    Q :BUFFER INTEGER RANGE 0 TO 7);
END counter3;
```

```
ARCHITECTURE behavior OF counter8 is
BEGIN
    PROCESS(CLK,CLR)
    BEGIN
        IF CLR = '0' THEN
            Q <= 0;
        ELSIF EBL = '0' THEN
            Q <= Q;
        ELSIF (CLK'EVENT AND CLK = '1';
            Q <= Q + 1;
        END IF;
    END PROCESS;
END behavior;
```


non- 2^N binary counter

- * Creation of the non- 2^N binary counter requires a test of the output state of the counter, followed by a reset to zero, if necessary. In a MOD-3 counter, for example, Qout takes values 0, 1, 2, 0, 1, 2,...
- * The code is written to reset the counter to zero whenever the counter has an output value of 2:
- * **Qout <= Qout +1;**
- * **IF Qout = 2 THEN**
Qout <= 0;

Mod 14 Up Counter

```
ENTITY count4up IS
  PORT(CLK: IN BIT;
        CLR: IN BIT;
        QOUT: BUFFER INTEGER RANGE 0 to 15);
END count4up;
ARCHITECTURE circuit OF count4up IS
  BEGIN
    PROCESS (CLK, CLR)
    BEGIN
      IF (CLR = '0') THEN QOUT <= 0;
      ELSIF (CLK'EVENT and CLK = '1') THEN
        QOUT <= QOUT + 1;
        IF QOUT = 13 THEN
          QOUT <= 0;
        END IF;
      END PROCESS;
    END circuit;
```

Test bench for counter

```
* UUT : MOD32COUNTER
```

```
* PORT MAP(CLK => CLK, CLR => CLR, EBL =>EBL, DIR => DIR,
```

```
* QOUT => QOUT );
```

```
* process
```

```
* begin
```

```
*     wait for 20ns;
```

```
*     if CLK ='0' then
```

```
*         CLK <= '1';
```

```
*     else
```

```
*         CLK <= '0';
```

```
*     end if;
```

```
* end process;
```

```
* EBL <= '0' AFTER 600ns, '1' AFTER 900ns;
```

```
* end Behavioral;
```

MOD-5 Binary Up-Counter With Enable and Clear

*** ENTITY counter5 IS**

PORT(

CLK :IN BIT;

Q :BUFFER INTEGER RANGE 0 TO 7);

END counter5;

ARCHITECTURE behavior OF counter5 is

BEGIN

PROCESS(CLK,CLR)

BEGIN

IF (CLK'EVENT AND CLK = '1') THEN

IF Q = 4 THEN

Q <= 0;

ELSE Q <= Q +1;

END IF;

END PROCESS;

END behavior;

MOD 5 Binary Up-Counter State Diagram

- * Unused states (counts 101, 110, and 111) feed the initial count (000). This is necessary so that if a counting error occurs, such as during power-on or in a noisy environment, the counter returns to the designed counting sequence.
- * One traditional method of building this counter would be to design a MOD 8 binary up-counter and use the decode of count 101 to drive the RESET input of the three counter flip-flops.
- * This means that the state 101 exists for a very small time, tens of nanoseconds, before resetting the counter back to 000.
- * A cleaner method for designing the MOD 5 counter is an approach that only has the five required states. This can be easily accomplished using VHDL.

Cascading Counters

- * There are some requirements in which counters must be used in stages. In many digital circuits, multiple clock frequencies are used.
- * This is a consequence of the fact that the power consumed by digital devices, particularly CMOS circuits, is directly proportional to the clock speed.
- * In a computer, for example, the central processing unit (CPU) usually runs in the GHz range, but communication channels can run in the MHz, or even kHz ranges.
- * Consider the arrangement shown below.

Cascaded Counters

